


PART – B

(5 x 13 = 65 Marks)

Q.No.	Questions	Marks	KL	CO
11. a)	State and explain KCL and KVL with examples.	13	K2	CO1

(OR)


b)	Calculate the equivalent resistance R_{ab} in the circuit shown below	13	K2	CO1
----	---	----	----	-----

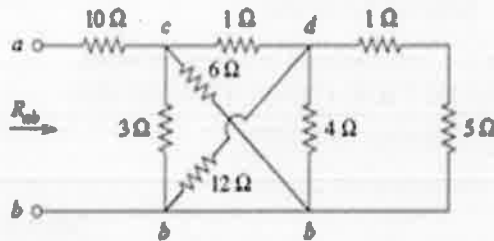

12. a)	State and explain Thevenin's theorem with an example.	13	K2	CO2
--------	---	----	----	-----

(OR)

b)	Using superposition theorem, find the voltage v_o for the circuit shown below.	13	K2	CO2
----	--	----	----	-----

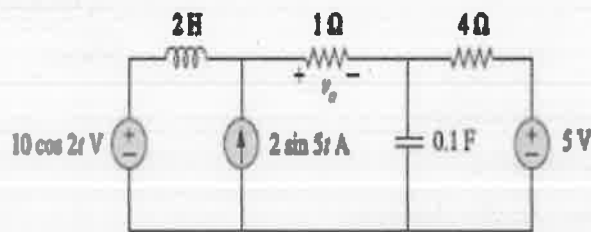

13. a)	Derive the following expressions for a series RLC i. Resonant frequency of the circuit ii. Q-Factor of the circuit at the resonant frequency iii. Bandwidth of the resonant circuit	13	K2	CO3
--------	--	----	----	-----


(OR)

b)	Derive the following expressions for a single tuned circuit (i) resonant frequency (ii) the output voltage at resonance.	13	K2	CO3
----	---	----	----	-----

14. a)	Derive the transient response of RL Circuit with excitation by step signal.	13	K2	CO4
--------	---	----	----	-----

(OR)

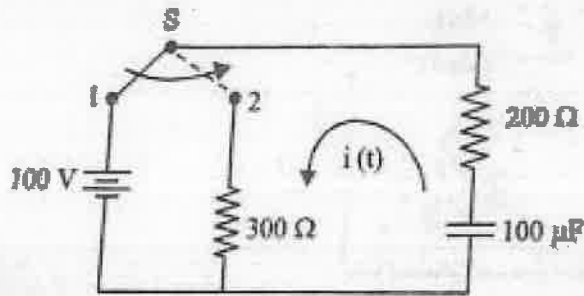- b) In the circuit shown below, switch s is in position 1 till steady state conditions are reached and the moved to 2. Find the energy dissipated in the two resistors. Show that this is equal to the energy stored in the capacitor before moving the switch.



15. a) With the necessary expressions, explain the Z and Y parameters for a two port network. 13 K2 CO5

(OR)

- b) Explain the transmission parameters for the two-port network. 13 K2 CO5

PART – C

(1 x 15 = 15 Marks)

- | Q.No. | Questions | Marks | KL | CO |
|--------|---|-------|----|-----|
| 16. a) | With an illustration, explain the concept of star to delta transformation and delta to star transformation. | 15 | K2 | CO1 |
| (OR) | | | | |
| b) | Determine the current I_o in the circuit shown below using Norton's theorem. | 15 | K2 | CO2 |

