

Reg.No.:



VIVEKANANDHA COLLEGE OF ENGINEERING FOR WOMEN
[AUTONOMOUS INSTITUTION AFFILIATED TO ANNA UNIVERSITY, CHENNAI]
Elayampalayam – 637 205, Tiruchengode, Namakkal Dt., Tamil Nadu.

Question Paper Code: 80030

B.E. / B.Tech. DEGREE END-SEMESTER EXAMINATIONS – JAN. / FEB. 2025

Second Semester

Electrical and Electronics Engineering

U23EE202 - ELECTRIC CIRCUIT THEORY

(Regulation 2023)

Time: Three Hours

Maximum: 100 Marks

Answer ALL the questions

Knowledge Levels (KL)	K1 – Remembering	K3 – Applying	K5 - Evaluating
	K2 – Understanding	K4 – Analyzing	K6 - Creating

PART – A


(10 x 2 = 20 Marks)

Q.No.	Questions	Marks	KL	CO
1.	State Kirchoff's laws.	2	K1	CO1
2.	Compare series and parallel circuit.	2	K1	CO1
3.	What is the condition for maximum power transfer?	2	K2	CO2
4.	Give the expression for star to delta transformation.	2	K1	CO2
5.	Define Resonance.	2	K2	CO3
6.	Define coefficient of coupling.	2	K1	CO3
7.	State the relationship between line and phase quantities of a 3 phase delta connected system	2	K2	CO4
8.	What are the advantages of 3 phase circuits over single phase circuits?	2	K2	CO4
9.	Define transient time.	2	K1	CO5
10.	Differentiate transient and steady state response.	2	K2	CO5

PART – B


(5 x 13 = 65 Marks)

Q.No.	Questions	Marks	KL	CO
11. a)	Find the current in 10ohm resistor by using KVL method.	13	K3	CO1

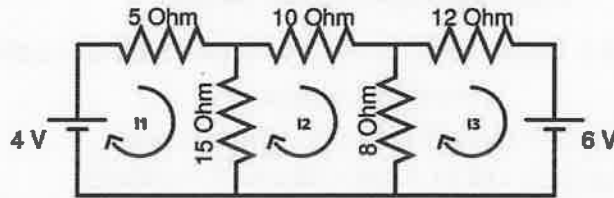


(OR)

b)	Determine current in 5ohm resistor by mesh analysis method.	13	K3	CO1
----	---	----	----	-----

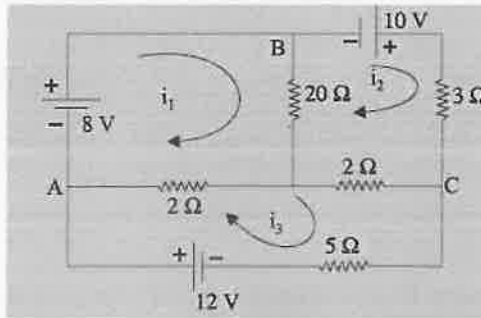


12. a)	Find the value of R such that maximum possible power will be transferred to R_L . Find also the value of the maximum power.	13	K3	CO2
--------	---	----	----	-----

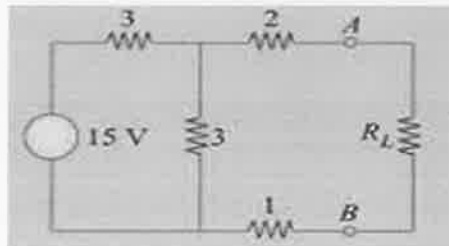

(OR)

b)	Find the current flowing through 20 Ω resistor using the superposition theorem.	13	K2	CO2
----	--	----	----	-----

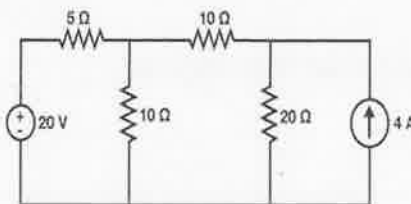

13. a) A series L-R-C circuit has a sinusoidal input voltage of maximum value 20 V. If inductance, $L = 0.03\text{H}$, resistance, $R = 5\ \Omega$, and capacitance, $C = 100\ \mu\text{F}$. Determine
- Resonant frequency and half power frequency (7)
 - Bandwidth and Quality factor. (6)

(OR)


- b) Derive the expression for mutual inductance of a coupled coils. 13 K2 CO3
14. a) A balanced three phase star connected load draws power from 440V supply. Two wattmeters indicates $W_1=4.2\text{kW}$ and $W_2=0.8\text{kW}$. Calculate
- Total power and power factor (8)
 - Current in the circuit (5)

(OR)

- b) Explain about Star and Delta connected three phase balanced circuits. 13 K2 CO4
15. a) Derive the expression for a transient response of a RC circuit for step input signal. 13 K2 CO5

(OR)

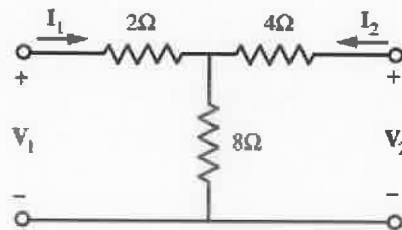- b) Find the hybrid parameters for the two-port network shown. 13 K2 CO5



PART - C

(1 x 15 = 15Marks)

- | Q.No. | Questions | Marks | KL | CO |
|--------|---|-------|----|-----|
| 16. a) | Explain in detail about the dot convention in coupled circuits. | 15 | K2 | CO3 |

(OR)

- | | | | | |
|----|---|----|----|-----|
| b) | The Q factor of a series resonant circuit at 50Hz is 1.5. If this circuit is supplied with a constant voltage and variable frequency, find frequency at which capacitor voltage is maximum. | 15 | K3 | CO3 |
|----|---|----|----|-----|